

Platformio

Shreyas Kumar

CONTENTS

I	Question	1
II	Solution	1
III	Truth Table	2
IV	Logical Diagram	2
V	Components	2
VI	Implementation	3

I QUESTION

A Boolean function F of three variables X , Y , and Z is given as

$$F(X, Y, Z) = (X' + Y + Z).(X + Y' + Z').(X' + Y + Z').(X' Y' Z' + X' Y Z' + X Y Z')$$

Which one of the following is true?

- $F(X, Y, Z) = (X + Y + Z).(X + Y' + Z').(X' + Y' + Z')$
- $F(X, Y, Z) = (X' + Y).(X + Y' + Z')$
- $F(X, Y, Z) = (X' Z') + (Y Z')$
- $F(X, Y, Z) = (X' Y' Z) + (X Y Z)$

II SOLUTION

$$\begin{aligned}
 F(X, Y, Z) &= (X' + Y + Z).(X + Y' + Z').(X' + Y + Z').(X' Y' Z' + X' Y Z' + X Y Z') \\
 &= (X' + Y + Z).(X + Y' + Z').(X' + Y + Z').(X' Z'.(Y + Y') + X Y Z') \\
 &= (X' + Y + Z).(X + Y' + Z').(X' + Y + Z').(X' Z' + X Y Z') \\
 &= (X' + Y + Z).(X + Y' + Z').(X' + Y + Z').(Z').(X' + X Y) \\
 &= (X' + Y + Z).(X + Y' + Z').(X' + Y + Z').(Z').(X' + Y) \\
 &= (X' + Y + Z).(X + Y' + Z').(X' + Y + Z').(Z').(X' + Y)
 \end{aligned}$$

Let $(X' + Y) = A$

$$\begin{aligned}
 F(X, Y, Z) &= (A + Z).(X + Y' + Z').(A + Z').(Z').(X' + Y) \\
 &= (X + Y' + Z').(A + Z Z').(Z').(X' + Y) \\
 &= (X + Y' + Z').(X' + Y).(Z').(X' + Y) \\
 &= (X + Y' + Z').(X' + Y).(Z') \\
 &= (X' + Y).(X Z' + Z' Y' + Z' Z') \\
 &= (X' + Y).(X Z' + Z' Y' + Z' Z') \\
 &= (X' + Y).(X Z' + Z' Y' + Z') \\
 &= (X' + Y).(Z').(X + Y' + 1)
 \end{aligned}$$

$$\begin{aligned}
 &= (Z').(XX' + X'Y' + X' + YX + YY' + Y) \\
 &= (Z').(X'Y' + X' + YX + Y) \\
 &= (Z').(X'.(Y' + 1) + Y.(X + 1)) \\
 &= (Z').(X' + Y)
 \end{aligned}$$


$$F(X, Y, Z) = Z'X' + Z'Y$$

III TRUTH TABLE

X	Y	Z	F
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

Truth table for Boolean function 'F'

IV LOGICAL DIAGRAM

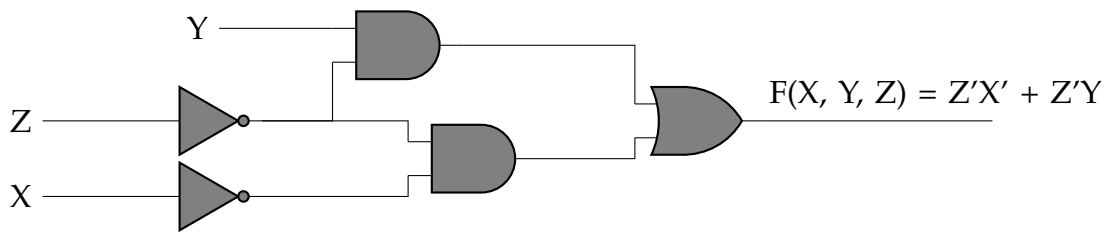

V COMPONENTS

Component	Values	Quantity
Arduino	UNO	1
Jumper Wires	M-M	10
Breadboard		1
LED		2
Resistor	220 ohms	1

List of items required

VI IMPLEMENTATION

Arduino PIN	INPUT	OUTPUT
2	X	
3	Y	
4	Z	
13		F

Connections

Procedure:

- Connect the circuit as per the above table.
- Connect the output pin to LED.
- Connect inputs to Vcc for logic 1, ground for logic 0.
- Execute the circuit using the below code.

<https://github.com/shr-eyas/FWC/blob/main/platformio.cpp>

- Change the values of X, Y, Z in the code and verify the truth table.